

PHY 338k Lab Report 1

Lily Nguyen with Anna Grove

September 18, 2025

1 Introduction

2 Lab 1: Basic measurements and oscilloscope use

2.1 Wiring inside the breadboard

2.2 Output impedance

2.2.1 Open circuit voltage

2.2.2 Closed circuit current

2.2.3 Output impedance

2.3 Voltage divider

2.3.1 Voltage divider circuit

2.3.2 General case voltage divider

2.4 Measuring voltage waveforms with an oscilloscope

2.4.1 Measuring the waveform from a function generator

2.4.2 Scope triggering

2.4.3 Square wave

2.4.4 Function generator output impedance

2.4.5 RMS amplitude

2.4.6 Rise time

3 Lab 2: RC Circuits

3.1 Circuit A

3.1.1 Rise and fall time

3.1.2 Integrator

3.1.3 Low-pass filter

3.2 Circuit B

3.2.1 Time constants

3.2.2 Differentiator

3.2.3 High-pass filter

3.3 Comparison with theory

3.3.1 Circuit A

3.3.2 Circuit B

2

4 Lab 3: Inductors and LC Filter Circuits

4.1 Impedance measurement with the LCR meter

4.2 Impedance measurements with an oscilloscope

4.3 Notch filter

assistance and feedback were invaluable in helping us understand the experimental procedures and circuit concepts. We also appreciate the department's laboratory facilities and equipment, which made these experiments possible.