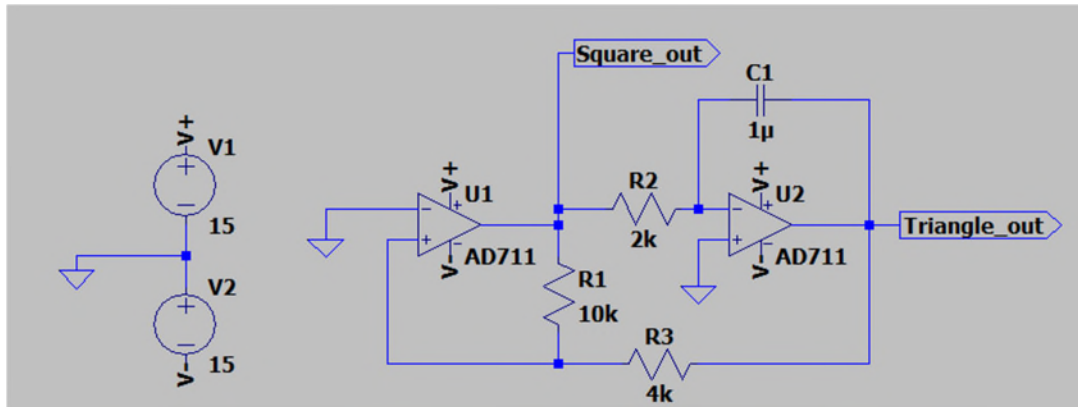


(a) Two op-amp triangle and square wave generator. The frequency of the wave can be changed by adjusting the value of R2 without changing the output amplitude.



(b) Example of a waveform shaping circuit to convert a triangle wave to a sine wave. This circuit is from the web site <https://sound-au.com/articles/sinewave.htm#s58>

